

Error Report

Format:

NUID (whatever is below is what you got wrong)

25K-0527

Q5

Minimum SOP's grouping done is incorrect you should get 1 8 cell and 1 4 cell group but I didn't penalize because of the simplification part me that error vaporized/got nullified as the final simplified exp was correct, if you do that in the exam Sir will deduct marks (can tell by experience)

Q7

part 1 incorrect

Q8

part b incorrect

Q10

part a minimum SOP incorrect

(outstanding work and presentation!!!)

25K-0578

Q2

no circuit drawn, I have not deducted marks although there were for the circuit, because of the statement you wrote, please if the question explicitly asks for something do that even if that is obvious, there is a reason why it is being asked for because examiner wants to see it and it carries marks

Q3

part 1 incorrect

Q5

part 2, 3, and 4 are incorrect

Q7

part 1 incorrect

Q10

part b incorrect

(outstanding work and presentation!!!)

25K-0819

Q1

part4 incorrect

Q4

part 1 and 2 (given full but you are not supposed to use as many gates, if you do that in the exam Sir will deduct marks (can tell by experience))

Q7

part 2 and 3 incorrect

Q10

part a minimum SOP and POS incorrect

25K-0772

Q2

no circuit drawn, I have not deducted marks although there were for the circuit, because of the statement you wrote, please if the question explicitly asks for something do that even if that is obvious, there is a reason why it is being asked for because examiner wants to see it and it carries marks

Q3

part 1 and 2 incorrect

Q5

all parts incorrect

Q7

part 1 incorrect

Q10

part b incorrect

25K-0708

Q3

all parts incorrect

Q5

because you expanded and solved logically it is sound and I've awarded full marks do cross check with sir on if he would accept a solution like this in the exam, because what most students and I too did back in my time was to draw gates without expanding, because that just increases the number of gates in the circuit

Q6

incorrect 1 mark lost for answer (silly mistake, but I had to be fair with everyone because of the marking key)

Q7

part a and 3 incorrect

25K-0515

Q2

given full but kindly for future note that if the question asks for something you are supposed to do it no matter how obvious it is

Q3

part i NOR implementation incorrect

Q5 incorrect

Q7

part 1 incorrect

Q10

part b incorrect

25K-0883

Q5

part a and b incorrect

Q10

part a incorrect

25K-0522

Q3

incorrect

Q4

part a

Q5

part b incorrect

Q8

part b

25K-0790

Q3 incorrect

Q4

incorrect

Q5

part b and d incorrect

Q6 incorrect

Q8

part b incorrect

Q10

part b incorrect

Mohaddisa Zehra (your name was used because the student ID didn't show on the NU ID email,
Sorry)

Q3)

part a and b incorrect

Q4

incorrect

Q5)

incorrect

Q7

part c incorrect

Q9

part b incorrect

25K-0803

Q1

part 2 and 3 incorrect part 4 missing

Q3

incorrect

Q4

part 1 NOT gate not permitted for usage in the problem statement

Q5

almost missing

Q6

missing

Q7

incorrect

Q8

incorrect

Q9

incorrect

Q10

part b incorrect

25K-0543 - P

Q2

question asked for 3 things

Q3

incorrect

Q4

part 1 incorrect

Q5

all incorrect but part a

Q8

part b incorrect

25K-0559

Q1

part 2,3, 4 incorrect

Q2

circuit missing

Q3

incorrect

Q4

part 1 incorrect

Q5

POS exp missing and part b incorrect

Q8

part b incorrect

25K-0561

Q1

part a, c incorrect

Q3

incorrect

Q4

incorrect

Q5

part d incorrect

Q8

part b incorrect

25K-0572

Q2

truth table missing

Q4

part 1 incorrect

Q5

part b incorrect , c, d, missing

Q8

part b incorrect

25K-0576

Q1

part 2 incorrect

Q4

incorrect

Q5

part b, c, d incorrect

Q8

part b, awarded full because logically it is correct but see try keeping the variables same as to what they were given in the question, some one who grades on logic won't deduct marks, but it's better to never give the marker a chance to deduct any marks

Q9

part b incorrect

Q10

part b missing

25K-0609

Q3

incorrect

Q4

part 1 incorrect

Q5

part b and c incorrect

Q8

part b incorrect

Q10

part a incorrect

25K-0653

Q1

part b incorrect

Q4

incorrect

Q5

part c, d incorrect, d is logically correct but NOT gates are not permitted in a NOR-NOR only implementation

Q8

part b, awarded full because logically it is correct but see try keeping the variables same as to what they were given in the question, some one who grades on logic won't deduct marks, but it's better to never give the marker a chance to deduct any marks

Q9

part b incorrect

Q10

incorrect

25K-0668

Q4

incorrect

Q5

part b incorrect

Q7

part b have a look at what was submitted, please be careful of that in the future. I can not assume what was supposed to be written when, awarded full marks regardless

part c incorrect

Q10

part b incorrect

25K-0684

Q3

incorrect

Q5

c, and d incorrect

Q8

part b incorrect

Q10

incorrect

25K-0691

Q3

incorrect

Q5

incorrect

Q9

part a incorrect

(outstanding work and presentation!!!)

25K-0692

Q3

incorrect

Q4

incorrect

Q5

part b and c incorrect

Q8

part b incorrect

25K-0710

Q3

incorrect

Q5

incorrect

Q7

part a incorrect

Q10

part b incorrect

25K-0722

Q1

part c ans is wrong but since it was a petty mistake ik you forgot to copy paste, I've awarded full

Q3

part 1 and 2 incorrect

Q5

incorrect

Q7

part a incorrect

25K-0724 - P

Q2

question asked for 3 things

Q3

incorrect

Q4

part 1 incorrect

Q5

all incorrect but part a

Q8

part b incorrect

25K-0742 - P

Q3

incorrect

Q4

incorrect

Q5

part a and b incorrect

Q6

incorrect

Q7

part c incorrect

25K-0784 - P

Q3

incorrect

Q4

incorrect

Q5

part a and b incorrect

Q6

incorrect

Q7

part c incorrect

Q10

part (ii) incorrect

25K-0807

Q3

incorrect

Q4

part 1 incorrect

Q5

part b and c incorrect

Q8

part b incorrect

25K-0810

Q5

incorrect

Q7

incorrect (I've deducted lesser marks than other for you because logically everything is fine but the answer, you've inverted every single variable, or have missed a term)

25K-0820

Q3

incorrect and missing parts

Q4

incorrect

Q5

part b, c, d incorrect

Q9

part b incorrect

Q10

incorrect

25K-0834

Q3

part b and d

Q5

incorrect

Q7

part a

Q10

part b incorrect

25K-0863

Q3

part b, c, d incorrect

Q4

NAND - NOR implementation is not you drawing 2 separate circuits 1 using each gate

Q5

incorrect

Q8

part b incorrect

Q10

incorrect

25K-0891

Q1

part d incorrect

Q4

incorrect

Q7

part c incorrect

Q9

part a and b incorrect

Q10

part a incorrect

(outstanding work and presentation!!!)

25K-0943

Q3

incorrect

Q4

incorrect

Q5

part a and b incorrect

Q7

part a incorrect

25K-0957

Q4

incorrect

Q5

part b and c incorrect

Q9

part b incorrect

Q8

part b, awarded full because logically it is correct but see try keeping the variables same as to what they were given in the question, some one who grades on logic won't deduct marks, but it's better to never give the marker a chance to deduct any marks

Q10

part b incorrect

25K-0948

Q3

incorrect

Q4

part a incorrect

Q5

incorrect

Q7

part b incorrect

Q8

part b incorrect

25K-0980

Q3

part 1 incorrect and part 2 missing

Q4

incorrect

Q5

incorrect and 1 part missing

Q8

part b partially solved awarded partial marks in accordance

25K-3054

Q3

part 1 incorrect

Q4

incorrect

Q5

incorrect

Q7

part a and b incorrect

Q10

part b incorrect